

Experiment-2

To design and analyze the circuit for Full adder and Full sub tractor using Logic Gates.

Full adder



- **Full Adder** is the **adder** which adds three inputs and produces two outputs.
- The first two inputs are A and B and the third input is an input carry as C-IN.
- The output carry is designated as C-OUT and the normal output is designated as S which is SUM.

MCQ

How many bit added by Full adder circuit.

- (a) 1
- (b) 2
- (c) 3
- (d) 4

Full Adder

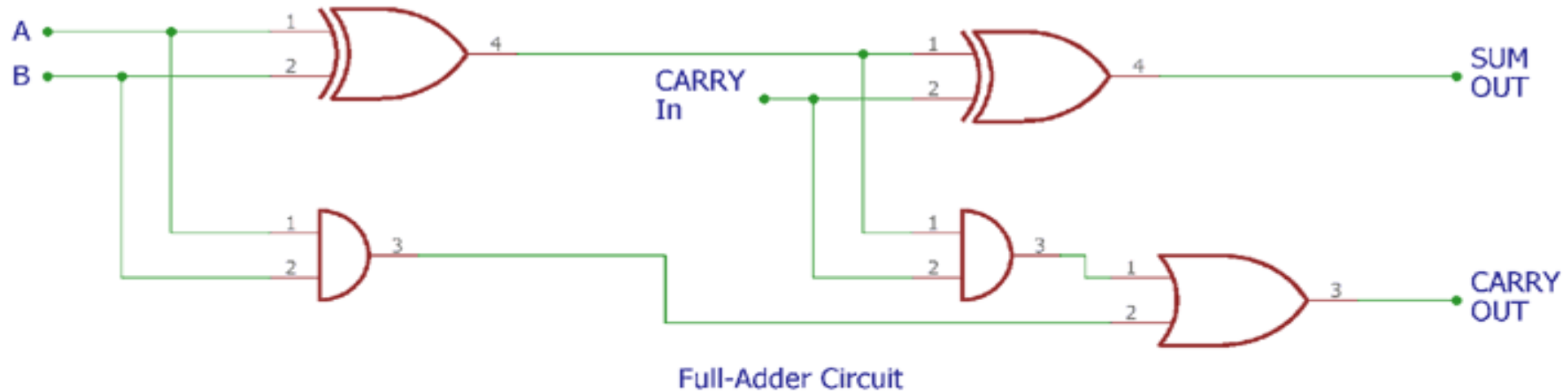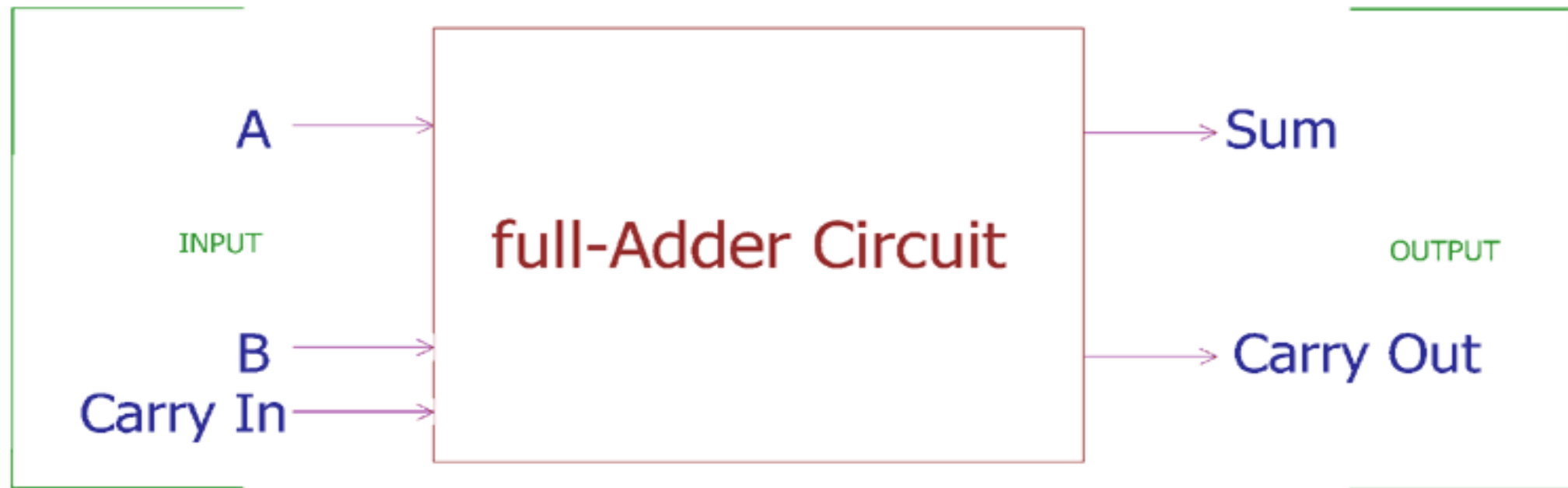

MCQ

XOR gate produces 1 out put when.....

- (a) All input zero
- (b) All input one
- (C) Both a and b
- (d) None of the above

MCQ

How many input and output in full adder circuit?


(a) 2, 2

(b) 3, 1

(c) 3, 2

(d) 3, 3

Symbol with truth table of full adder

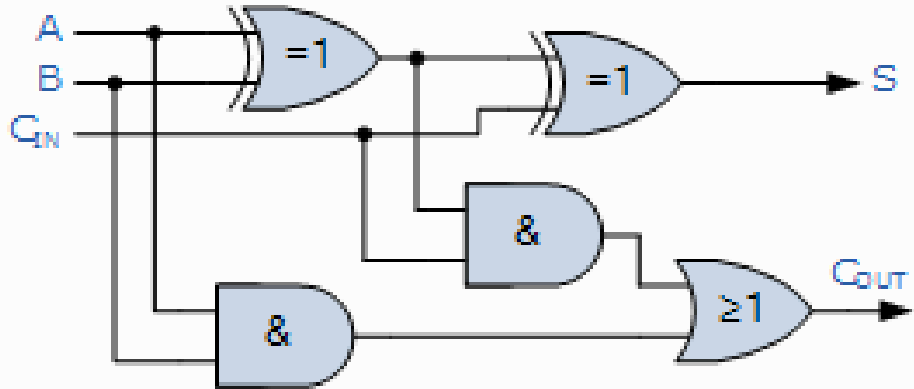Symbol	Truth Table				
	C-in	B	A	Sum	C-out
	0	0	0	0	0
	0	0	1	1	0
	0	1	0	1	0
	0	1	1	0	1
	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
	1	1	1	1	1

Which IC number for X-OR gate.

- (a) 7432
- (b) 7468
- (c) 7486
- (d) 7423


Bread Board Connection

Draw Bread Board Connection diagram:

VCC



Outputs

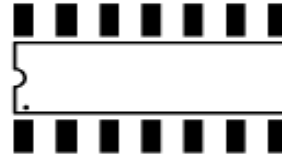


GND



Inputs


Full Adder Circuit Diagram

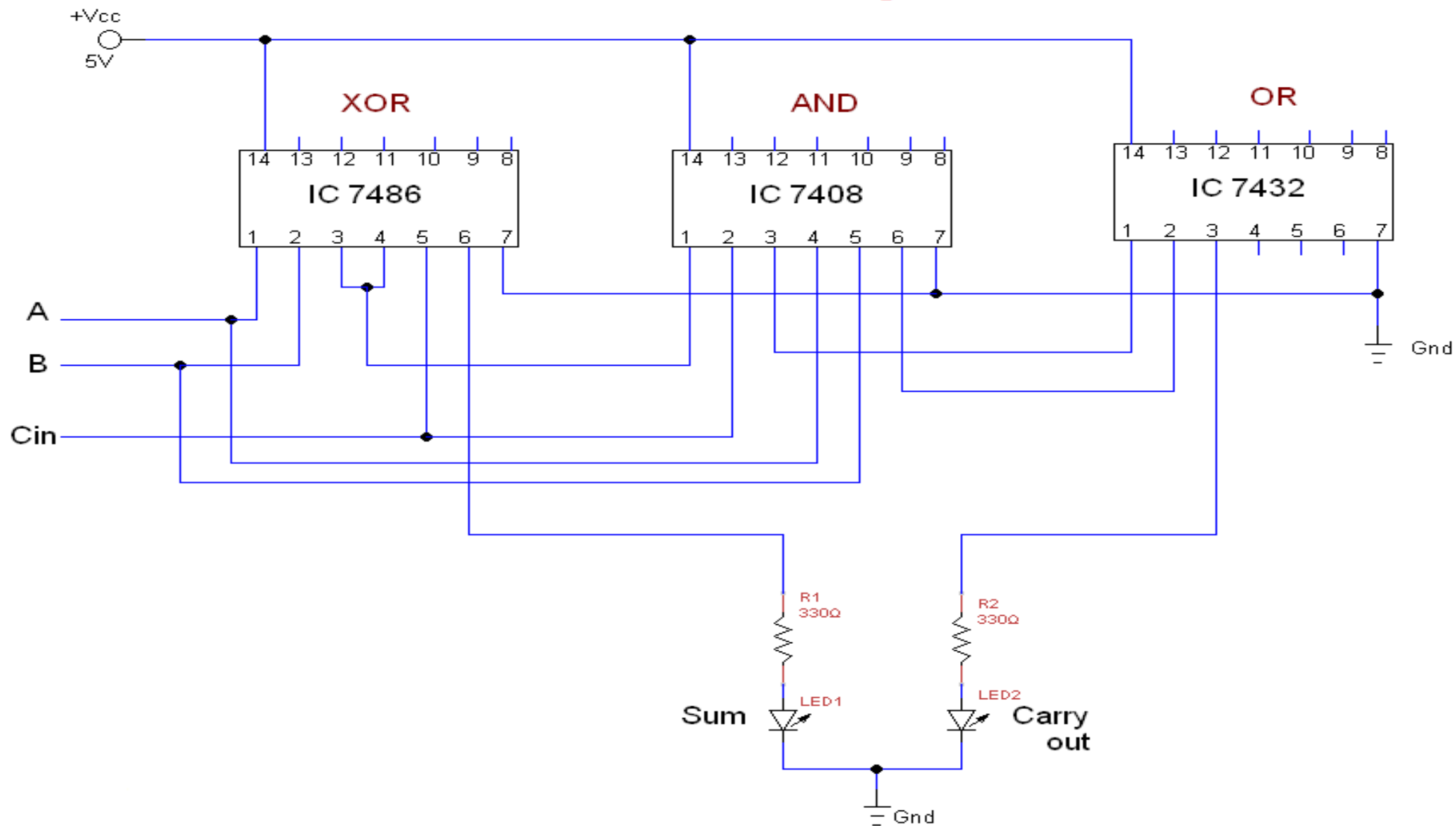

Full Subtractor

- The **full subtractor** is a combinational circuit which is used to perform subtraction of three input bits: the minuend , subtrahend , and borrow in .
- The **full subtractor** generates two output bits: the difference and borrow out .

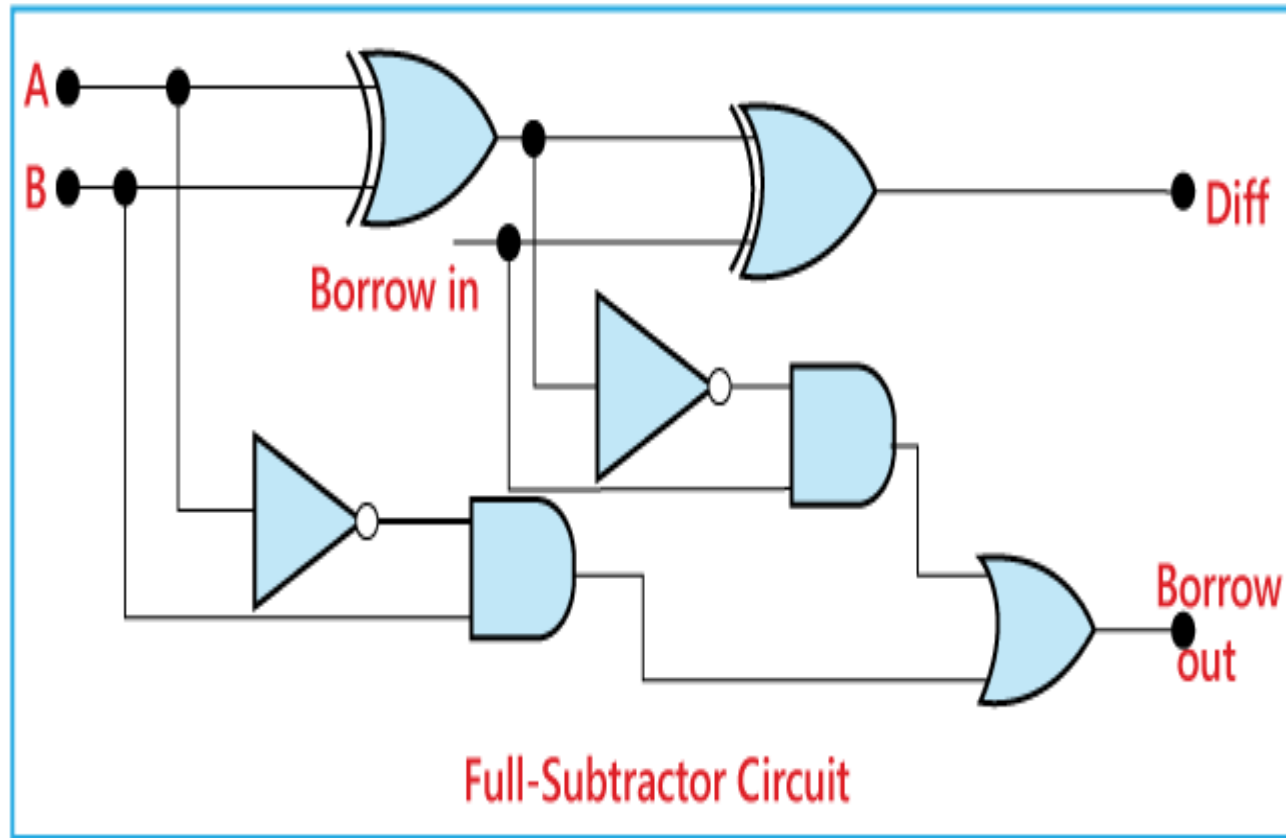Symbol with truth table of full subtractor






A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Draw Bread Board Connection diagram:

VCC



Outputs

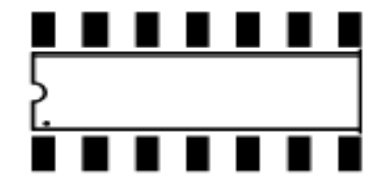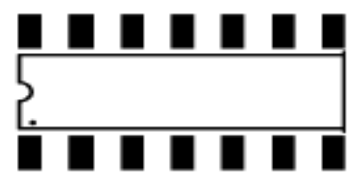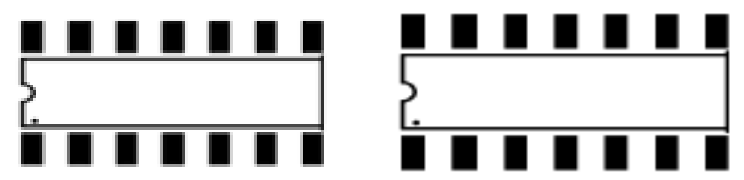

GND



Inputs

