
 
 


UNIT VI: ECE 213

PLA and PAL


Programmable Logic Array(PLA)

 - It has programmable AND array and programmable OR array.
- Because both arrays are programmable, it is flexible.
- The PLA is similar in concept to the PROM, except that the PLA does not provide full decoding of the variables and does not generate all the minterms.



- In PLAs, instead of using a decoder as in PROMs, a number (k) of AND gates is used where $k < 2^n$, (n is the number of inputs).

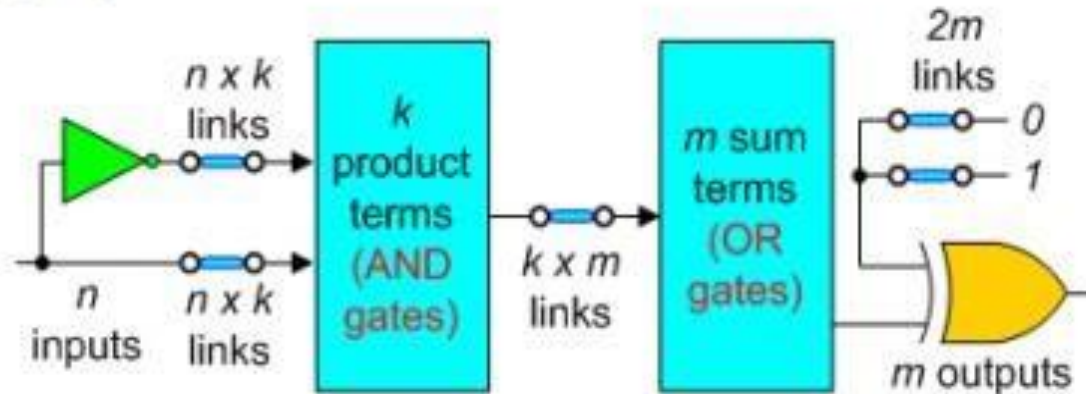A block diagram of the PLA is shown in the figure. It consists of n inputs, m outputs, and k product terms.



The product terms constitute a group of k AND gates each of $2n$ inputs.

Links are inserted between all n inputs and their complement values to each of the AND gates.

- The output of the OR gate goes to an XOR gate, where the other input can be programmed to receive a signal equal to either logic 1 or logic 0.
- The output is inverted when the XOR input is connected to 1 (since $x \text{ XOR } 1 = \neg x$).
- The output does not change when the XOR input is connected to 0 (since $x \text{ XOR } 0 = x$).

Example 1: Implement the following table using PLA.

A	B	C	F1	f2
0	0	0	1	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

Step 1: K-maps for simplification:

BC A		B			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

$$F_1 = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$

$$\overline{F}_1 = AB + AC + BC$$

BC A		B			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$$

$$\overline{F}_2 = \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C}$$

- Designing using a PLA, a careful investigation must be taken in order to **reduce the distinct product terms**.
- **Both the true and complement forms** of each function should be **simplified** to see which one can be expressed with **fewer product terms** and which one provides **product terms that are common** to other functions.

- K-maps for simplification:

BC A		B			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

$$F_1 = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$

$$F_1 = AB + AC + BC$$

BC A		B			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$$

$$F_2 = \overline{A}C + \overline{A}B + A\overline{B}\overline{C}$$


The combination that gives a minimum number of product terms is:

$$F_1' = AB + AC + BC \text{ or } F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$


This gives only 4 distinct product terms: AB , AC , BC , and $A'B'C'$.

Step 2: Logic Design

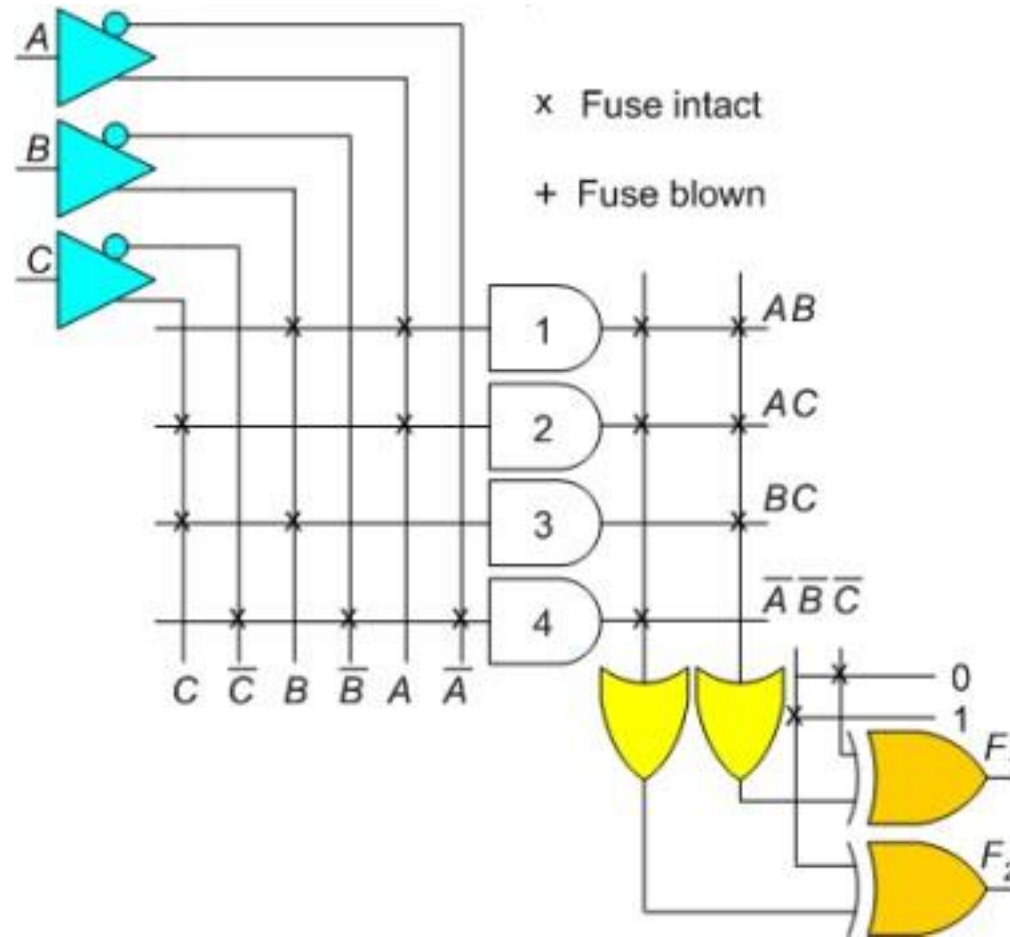


Programmable Array Logic (PAL)

 
- It has programmable AND array and fixed OR array.
- Because only the AND array is programmable, it is easier to use
- However, it is not flexible as compared to Programmable Logic Array (PLA).



(a) Programmable read-only memory (PROM)

 



(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

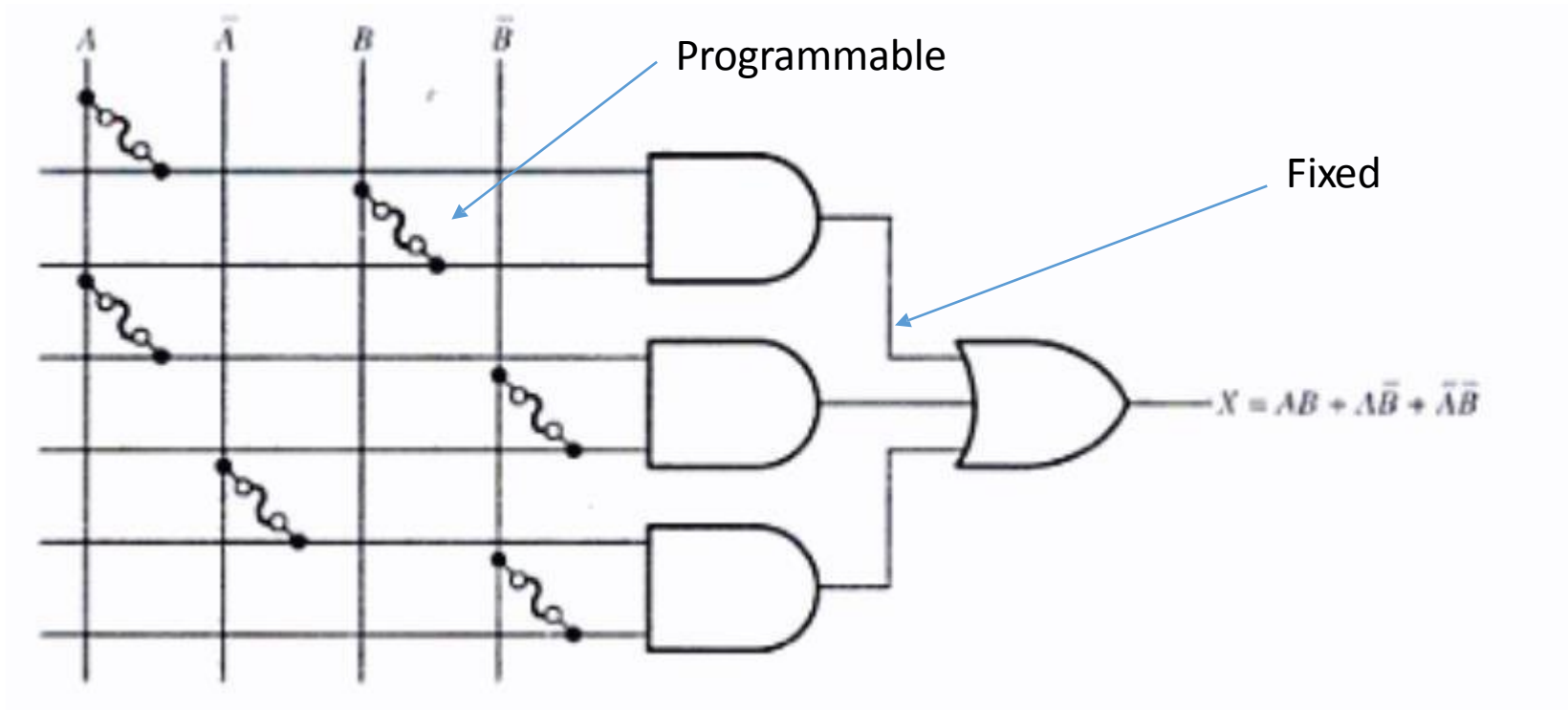Example 1: Implement $AB + A\bar{B} + \bar{A}B$ using PAL?



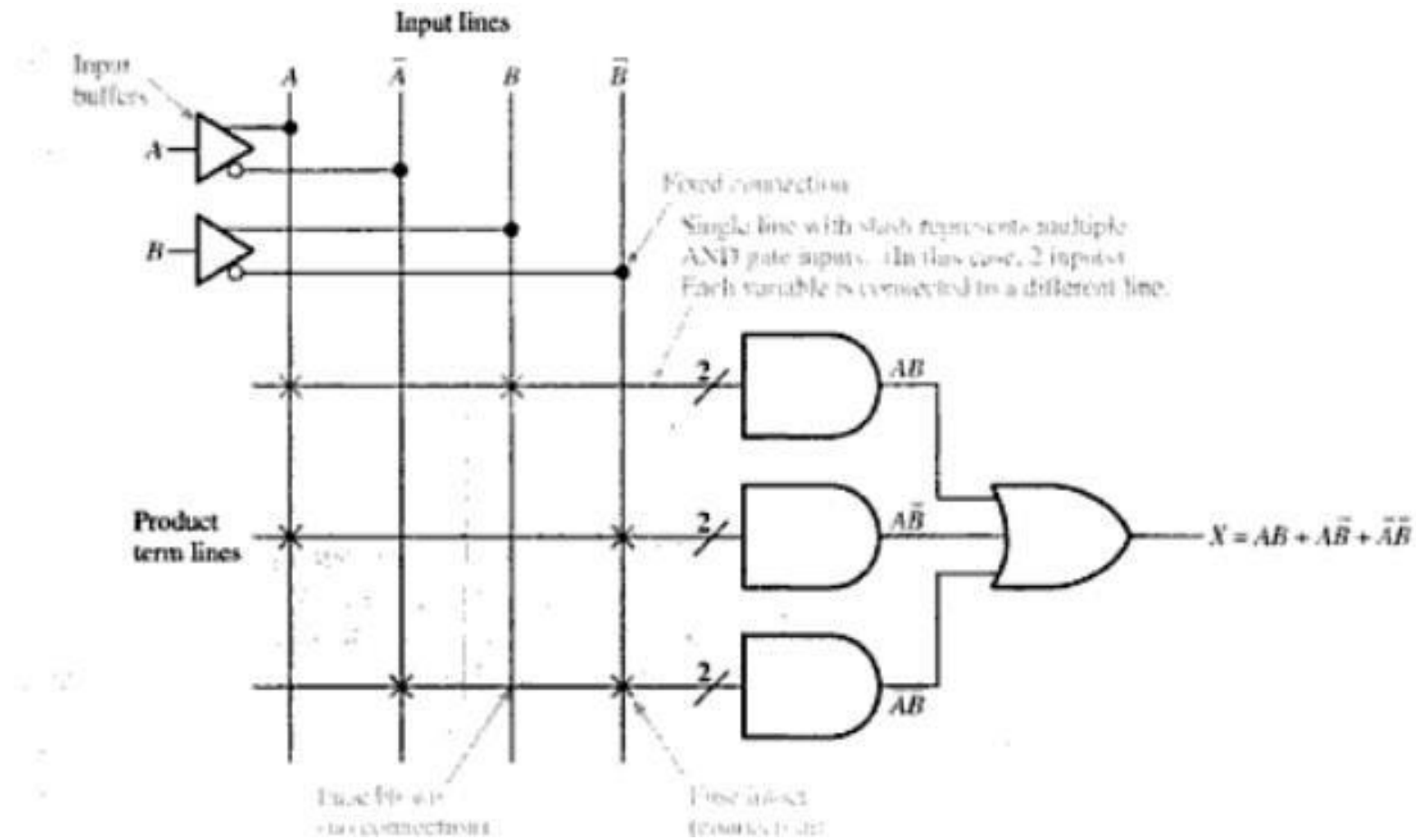

Simplified Diagram

Example 2:

Implement following function using PAL?

$$w(A, B, C, D) = \Sigma(2, 12, 13)$$

$$x(A, B, C, D) = \Sigma(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \Sigma(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \Sigma(1, 2, 8, 12, 13)$$

Sol:

Use K-map for Simplification

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$

Simplifying the four functions to a minimum number of terms results in the following Boolean functions:

$$w = ABC' + A'B'CD'$$


$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

LOGICAL DIAGRAM for PAL:

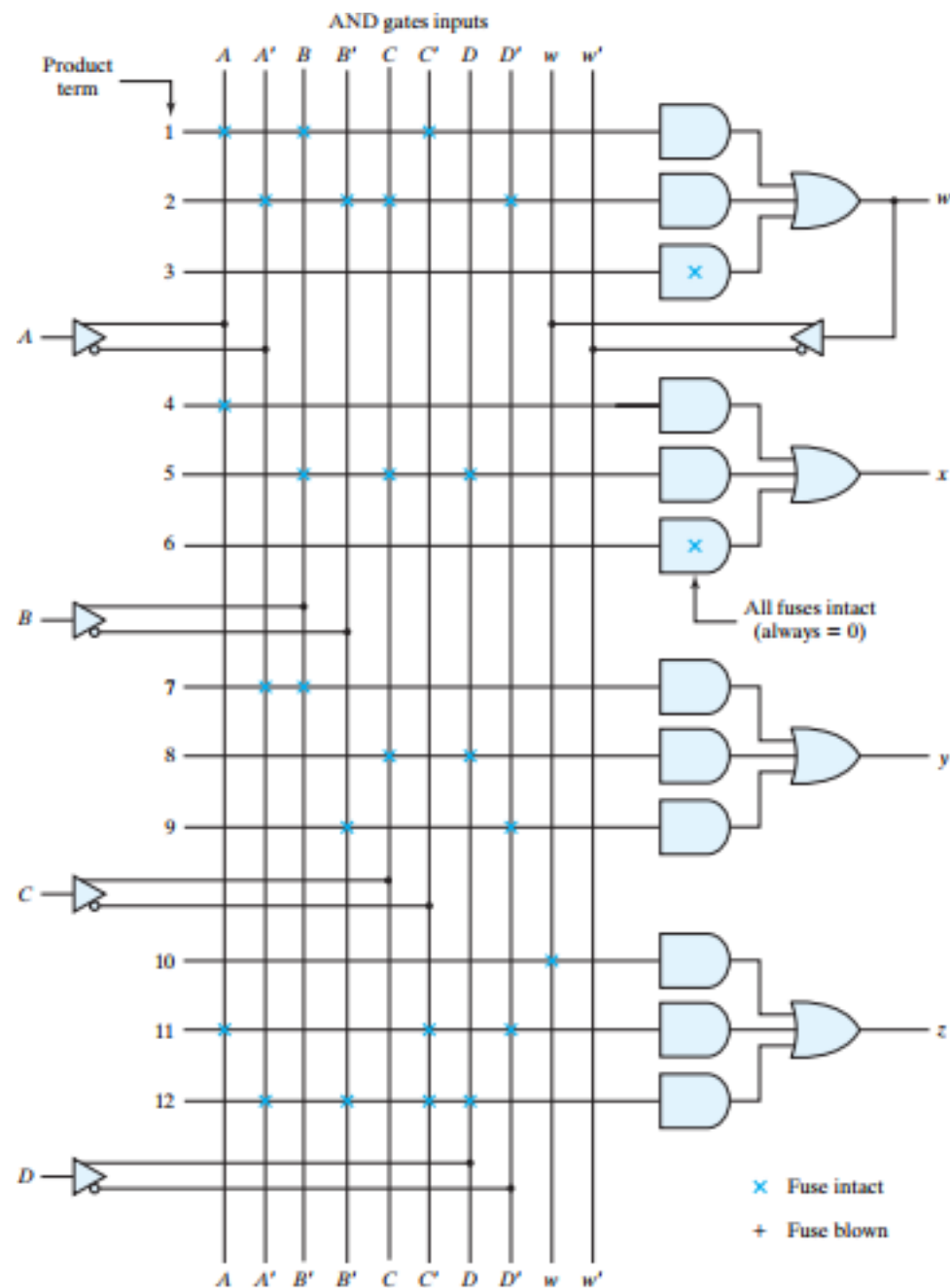

MCQ

PLAs, CPLDs, and FPGAs are all which type of device?

- A. SLD
- B. PLD
- C. EPROM
- D. SRAM

MCQ

PAL refers to

- a) Programmable Array Loaded
- b) Programmable Logic Array
- c) Programmable Array Logic
- d) None of the Mentioned

MCQ

PLD contains a large number of

- a) Flip-flops
- b) Gates
- c) Registers
- d) All of the Mentioned